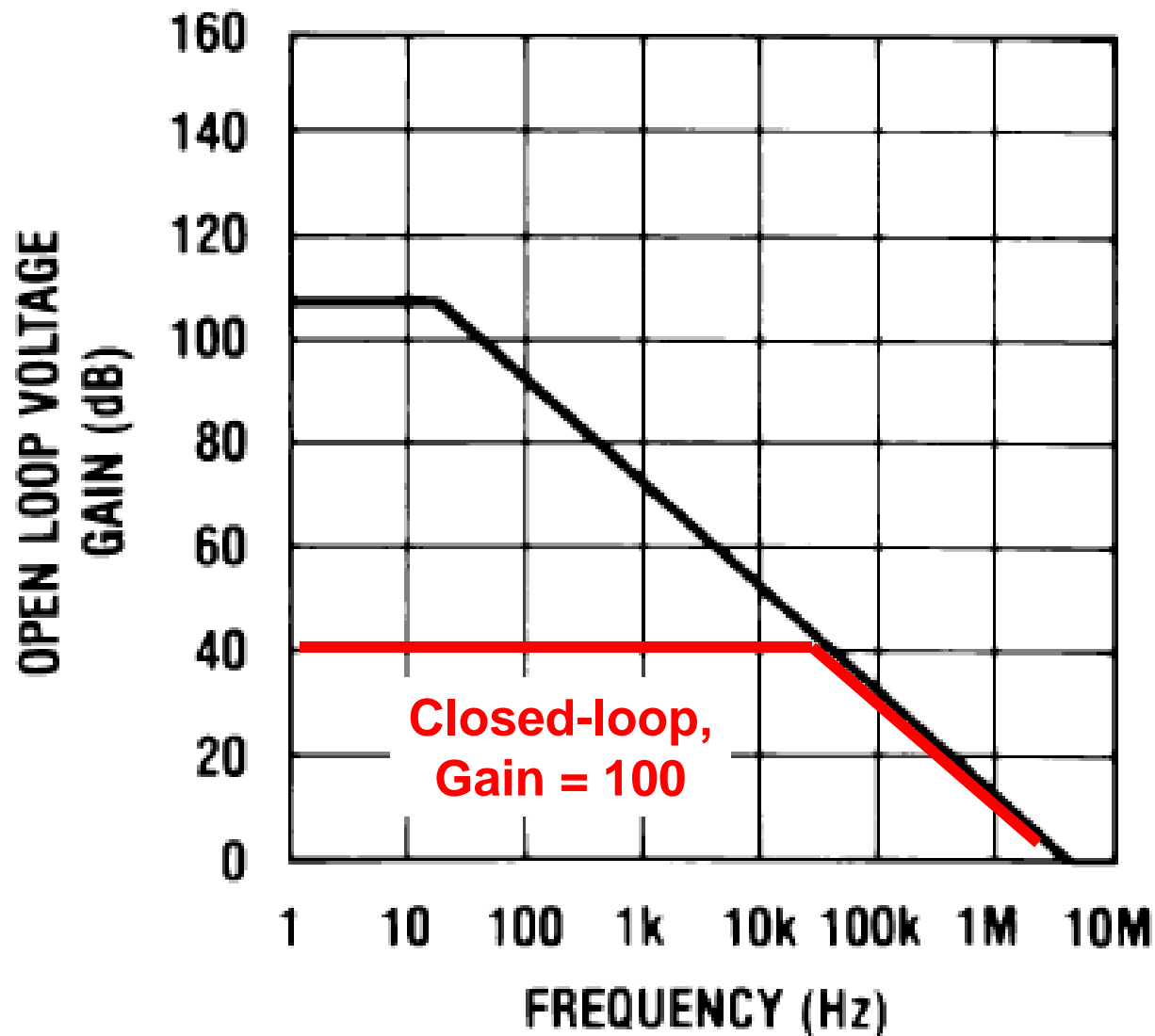


Ideal op-amp has the following characteristics:

1. Input impedance = infinity
2. Output impedance = 0
3. Voltage gain = infinity
4. Common-mode voltage gain = 0
5. $V_{\text{out}} = 0$ when both inputs are at the same voltage (i.e. zero “offset voltage”)
6. Output can change instantaneously (infinite slew rate)


Open-loop gain for LF411



Electronics Review


Kirchhoff's Laws

Energy is conserved

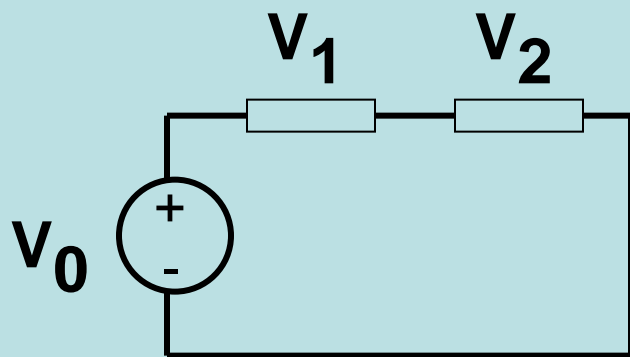


$$V_0 + V_1 + V_2 = 0$$

Charge is conserved

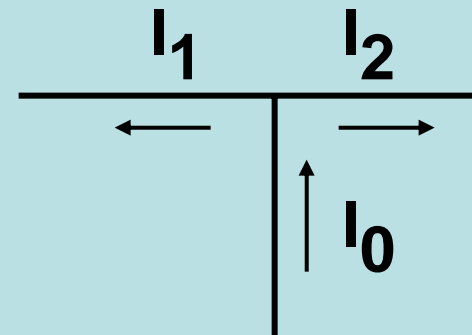

$$I_0 = I_1 + I_2$$

Impedances Model

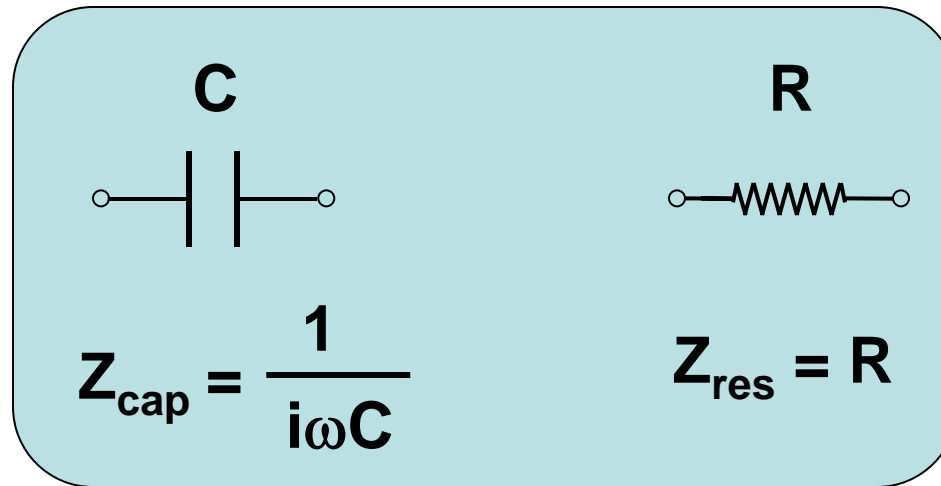


Differential Equation -> Algebraic Equation -> Impedance Model

$e^{i\omega t}$ is an eigenvector of $\frac{d}{dt}$


Substitute $V = V_o e^{i\omega t}$
 $I = I_o e^{i\omega t}$ into element relations

$$V = iR$$
$$i = C \frac{dv}{dt}$$

Impedances behave like resistors

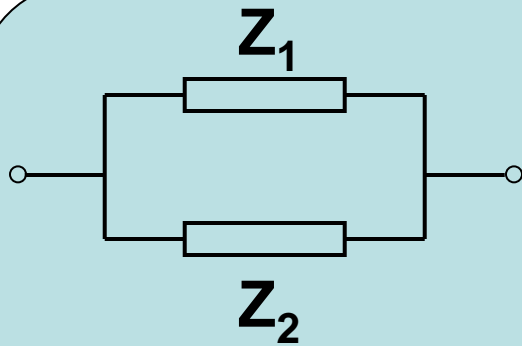

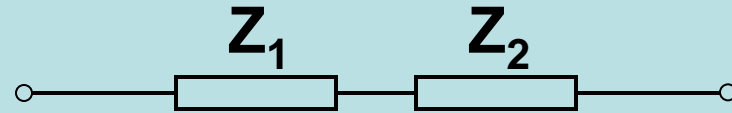
$$Z_{\text{parallel}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$



$$Z_{\text{series}} = Z_1 + Z_2$$

The Divider:

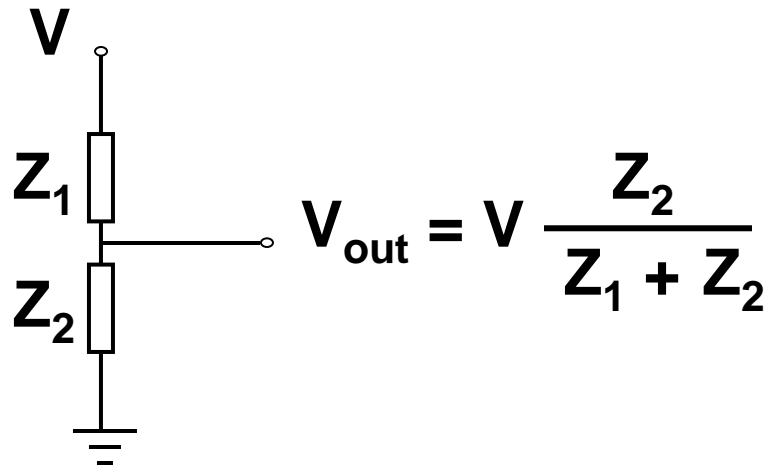


$$V_{\text{out}} = V \frac{Z_2}{Z_1 + Z_2}$$

Input and Output Impedances


$$(Z_{\text{output of Stage 1}}) \ll (Z_{\text{input of Stage 2}})$$

Example:

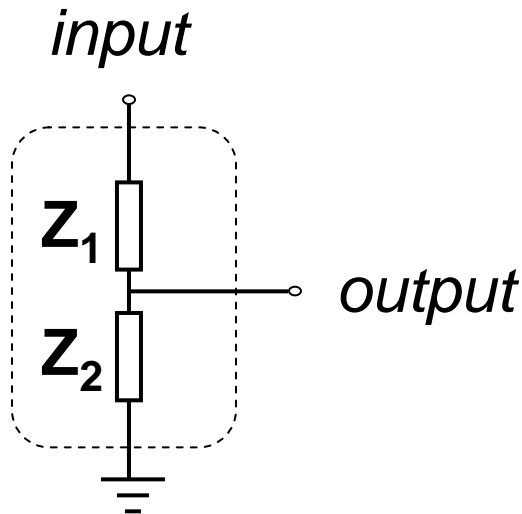

Input impedance: $Z_{\text{input}} = Z_1 + Z_2$

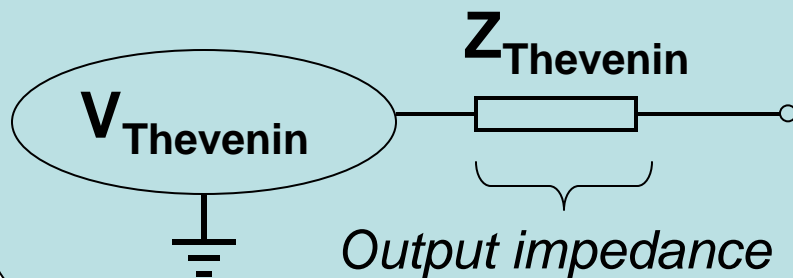Output impedance: $Z_{\text{output}} = \frac{Z_1 Z_2}{Z_1 + Z_2}$




V_{thev} = Open circuit output voltage

Z_{thev} = Open circuit resistance

($V_{\text{source}} = \text{short}$; $i_{\text{source}} = \text{open}$)

Op-Amps

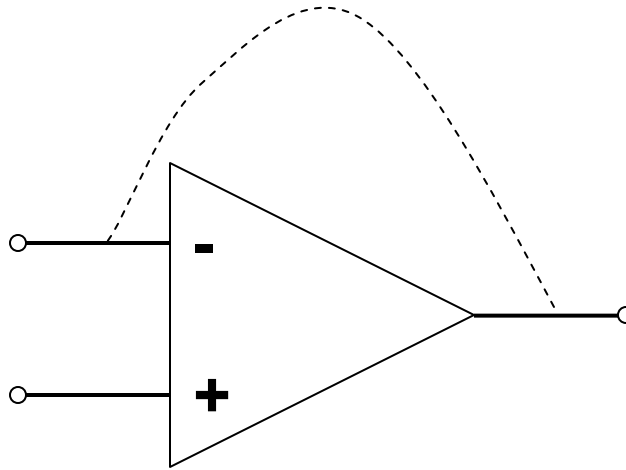

Two golden rules:

1. No current flows in
2. Output does whatever it takes to make $V^+ = V^-$

Nearest Neighbor (NN) model for nucleic acids

Assumes that the stability of a given base pair depends on the identity and orientation of neighboring base pairs.

There are 10 NN dimer duplexes:

Sequence	ΔG_{37° (kcal/mol)
	Unified (ref. 22)
AA/TT	-1.00
AT/TA	-0.88
TA/AT	-0.58
CA/GT	-1.45
GT/CA	-1.44
CT/GA	-1.28
GA/CT	-1.30
CG/GC	-2.17
GC/CG	-2.24
GG/CC	-1.84
Average	-1.42
Init. w/term. G•C*	0.98
Init. w/term. A•T*	1.03
Sodium concentration, M	1.0

Example:

5'-CA-3' paired with **3'-GT-5'**
is represented at **CA/GT**

SantaLucia, *PNAS* **95** 1998.

Nearest Neighbor (NN) model for nucleic acids

Total free energy,


Free energy from 10 possible NN

$$\Delta G^\circ(\text{total}) = \sum_i n_i \Delta G^\circ(i) + \underbrace{\Delta G^\circ(\text{init w/term G}\cdot\text{C}) + \Delta G^\circ(\text{init w/term A}\cdot\text{T})}_{\text{Initiation parameters (terminal GC or AC)}}$$

Initiation parameters (terminal GC or AC)

Initiation parameters account for sequence independent effects (e.g. terminal/internal NNs and counterion condensation)

Biochemistry: SantaLucia

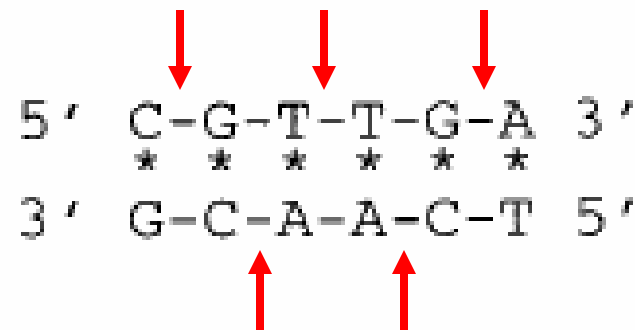

$$\begin{aligned}\Delta G^{\circ}_{37}(\text{pred.}) &= \Delta G^{\circ}(\text{CG/GC}) + \Delta G^{\circ}(\text{GT/CA}) + \Delta G^{\circ}(\text{TT/AA}) \\ &\quad + \Delta G^{\circ}(\text{TG/AC}) + \Delta G^{\circ}(\text{GA/CT}) + \Delta G^{\circ}(\text{init.}) \\ &= -2.17 - 1.44 - 1.00 - 1.45 - 1.30 + 0.98 + 1.03\end{aligned}$$

$$\Delta G^{\circ}_{37}(\text{pred.}) = -5.35 \text{ kcal/mol}$$

$$\Delta G^{\circ}_{37}(\text{obs.}) = -5.20 \text{ kcal/mol}$$

FIG. 1. Application of the unified nearest neighbor parameters (Table 1) and Eq. 1 to predict ΔG°_{37} . Each arrow points to the middle of one of the NN dimers. The duplex CGTTGA·TCAACG is non-self-complementary and thus $\Delta G^{\circ}(\text{sym})$ is zero.

SantaLucia, *PNAS* **95** 1998.

Table 2. Unified oligonucleotide ΔH° and ΔS° NN parameters in 1 M NaCl (22)

Sequence	ΔH° kcal/mol	ΔS° cal/k·mol
AA/TT	-7.9	-22.2
AT/TA	-7.2	-20.4
TA/AT	-7.2	-21.3
CA/GT	-8.5	-22.7
GT/CA	-8.4	-22.4
CT/GA	-7.8	-21.0
GA/CT	-8.2	-22.2
CG/GC	-10.6	-27.2
GC/CG	-9.8	-24.4
GG/CC	-8.0	-19.9
Init. w/term. G·C	0.1	-2.8
Init. w/term. A·T	2.3	4.1
Symmetry correction	0	-1.4

Oligomer

ΔH (kJ/mol)

ΔS (kJ/mol-K)

5'-ATAGC-3'
3'-TATCG-5'


-169

-0.483


5'-ATAGCATAGC-3'
3'-TATCGTATGC-5'

-336

-0.919

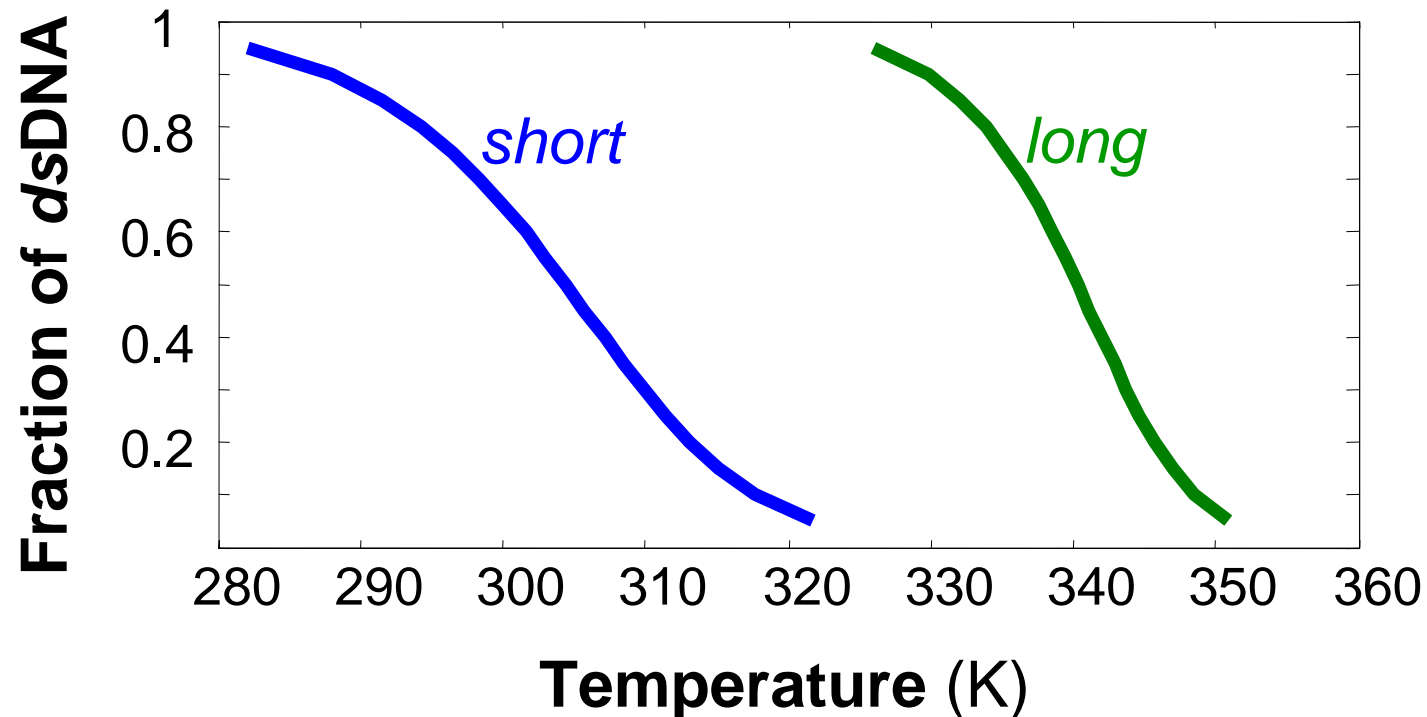

SYBR green

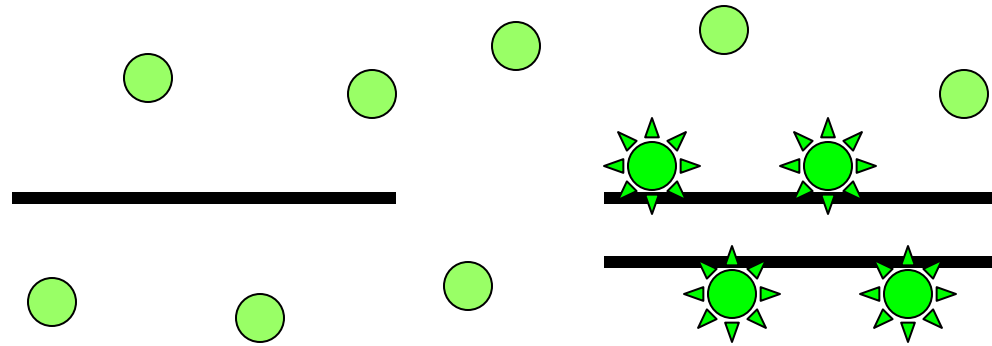

The fluorescence intensity of SYBR Green is enhanced over 100-fold on binding to DNA which results in bright fluorescent DNA bands against a very dark background

Using a transilluminator, it is possible to detect less than 100 pg of SYBR Green-stained DNA by eye and tens of picograms using a CCD system.

20.309 Experimental Setup

